Fire Alarm Circuit Using IC 555 Timer

COMPONENT:

- 2x 10K resistor
- 1x NE555
- 1x IR infrared sensor arduino
- 1x Pezo buzzer
- 1x 3mm led
- 1x 470 ohm resistor

BLOCK / CIRCUIT DIAGRAM:

